

M.Sc. (Physics) (CBCS Pattern) Sem-I
PSCPHYT03 - Paper-III - Core-III : Electronics

P. Pages : 2

Time : Three Hours



GUG/W/22/11181

Max. Marks : 80

- Notes : 1. All questions are compulsory.
2. All questions carry equal marks.

Either:

1. a) How Schottky diodes are constructed? Compare the characteristics of Schottky diode and p-n junction rectifier diode. **4+4**
b) What is biasing of a transistor? Discuss different methods of transistor biasing. **8**

OR

- e) What is quantum mechanical tunnelling in tunnel diode? Explain their V-I characteristics of tunnel diode. **8**
f) Explain construction and working of n-channel JFET. **6**
g) Write a short note on Q-Point of a transistor. **2**

Either:

2. a) With a neat diagram explain the action of Colpitts Oscillator. **8**
b) Explain direct-coupled amplifier. What are the advantages and disadvantages of it? **8**

OR

- e) What is a clipper? Describe: **8**
i) Positive Clipper ii) Biased Clipper iii) Combination Clipper
f) Explain the concept of voltage regulation. **8**
Explain with suitable circuit diagram working of Zener voltage regulator.

Either:

3. a) What is full adder? Give its truth table and draw the circuit of full adder using XOR gate. **8**
b) Describe the working JKMS ff with the help of logic diagram and draw the timing diagram for it. **8**

OR

- e) What is a shift register? What are the various types of shift registers? Explain the working of SISO shift register. **8**
f) With the help of neat diagram explain the working of R-2R ladder network DAC. **6+2**
Calculate the output voltage V_{out} of R-2R ladder type DAC when the input is 1000.

Either:

4. a) i) Describe frequency modulation. 2
- ii) Derive formula for instantaneous value of FM voltage. 4
- iii) Calculate the modulation index for an FM signal in which the modulating frequency is 2 kHz and the maximum deviation is 10 kHz. 2
- b) Draw the schematic diagram of reflex klystron. 8
Explain how bunching takes place in the klystron amplifier around the electron which passes the buncher cavity gap when the gap voltage is zero and becoming positive.

OR

- e) i) Describe phase modulation. Explain difference between FM and PM. 4
- ii) 100 kw carrier is modulated with 2kHz audio signal. 4
After modulation power in the carrier increases to 132 kw. Calculate modulation index.
- f) Draw and explain transistor AM modulator circuit. 8
5. All questions are compulsory.
- a) What is a photodiode? How does photodiode work? 4
- b) Explain the working of two-input transistor AND gate. 4
- c) Explain the use of OPAMP as a non-inverting amplifier. 4
- d) Audio signal of frequency 200 Hz is used to modulate a carrier of 500 kHz. Calculate band width and side frequencies. 4
