

**PSCPHYT11-4 - Paper-XI - Core Elective E1.4 : Applied Electronics-I Paper-II**

P. Pages : 2

Time : Three Hours



**GUG/W/22/11301**

Max. Marks : 80

---

- Either :
1. a) Draw the block diagram of a typical operational amplifier and explain the function of each block. **5**
- b) Discuss the open loop configuration of operational amplifier. **3**
- c) What is multivibrator? Compare monostable and astable multivibrators with suitable circuit diagrams. **8**

**OR**

- e) State Barkhausen criterion for oscillations. Draw circuit diagram for phase shift oscillator, explain its working and obtain the frequency of the oscillator. **8**
- f) Explain OP-AMP with negative feedback. discuss the effect of feedback on close loop gain and bandwidth. **8**

Either :

2. a) Discuss Fresnel zone problem and ground reflection with respect to microwave communication. **8**
- b) Explain the atmospheric effect on the propagation of microwaves. Discuss the use of antennas in microwave communication system. **8**

**OR**

- e) What is Modulation? Explain amplitude modulation. **8**
- f) What is Demodulation? Explain demodulation of AM waves. **8**

Either :

3. a) Draw the pin diagram of IC8085 microprocessor and labels all pins clearly. **8**
- b) What is mean by microprocessor? Explain about stack and subroutines. **8**

**OR**

- e) What are read only memory and random access memory? Explain their any three applications. **8**
- f) Explain the need of A/D and D/A converters. Explain the working of R-2R ladder D/A converter with suitable diagram. **8**

- Either :
4. a) What are magnetrons? Explain the principle of operation of magnetrons. 8
- b) Explain the working of Helix travelling wave tubes. 8

**OR**

- e) What is gunn effect? Explain principle operation of gunn diode. 8
- f) What are microwave devices? Explain klystrons used as microwave devices. 8
5. Attempt all the followings.
- a) Discuss LC tunable oscillator. 4
- b) Discuss fading sources. 4
- c) Explain assembly language programmes. 4
- d) Write on IMPATT diode and TRAPATT diode. 4

\*\*\*\*\*